Cyclic Codes

Definition: A linear code is called a cyclic code if every cyclic shift of a codeword is also a codeword. Thus, if , $a=[a_{n-1}, a_{n-2}, \ldots, a_0]$ is the codeword of the cyclic code of length n, then the cyclic shift of this codeword = $[a_{n-2}, a_{n-3}, \ldots, a_0, a_{n-1}]$ is the codeword of the same code. Shifting all bits to the left one position yield another codeword as $[a_{n-3}, a_{n-4}, \ldots, a_0, a_{n-1}, a_{n-2}]$.

Generation of Cyclic codes:

a. **Non-Systematic cyclic codes:** the output code word is generated using polynomial multiplication.

Procedure:

 For [D]=[a₁, a₂, a_k] data word, write the data word in terms of a power of a dummy variable and with a₁ weighted as MSB (Most Significant Bit) and a_k as LSB (Least Significant Bit).

i.e. $D(X)=a_k+a_{k-1}X+a_{k-2}X^2+\dots+a_1X^{k-1}$

where (+) is mod-2 addition EX-OR

for example if [D]=[11101] then $D(X)=1+X^2+X^3+X^4$

If $D(X)=1+X^2+X^6$ then [D]=[1000101]

 Multiplication: Multiply D(X) by what is called generator polynomial g(X) of order r. This g(X) is one of the factors of Xⁿ+1.

For example, if n=7, then $X^7+1=(X+1)(X^3+X^2+1)(X^3+X^2+1)$

For n=7, r=3, we can choose either $g(X) = X^3 + X^2 + 1$ or $X^3 + X+1$.

3. The output code words will be C(X)=D(X)g(X) then C(X) is used to find the output code word [C].

Ex: Write down the code table for the (7,4) non systematic cyclic code with generator polynomial $g(X) = X^3 + X + 1$.

Sol:

K=4, r=3 then D=[$a_1 a_2 a_3 a_4$] so the code table will be:

a 1	\mathbf{a}_2	a 3	a 4	c ₁	C ₂	C 3	C4	C 5	C 6	C 7	Wi
0	0	0	0	0	0	0	0	0	0	0	
0	0	0	1	0	0	0	1	0	1	1	3
0	0	1	0	0	0	1	0	1	1	0	3
0	0	1	1	0	0	1	1	1	0	1	4
0	1	0	0	0	1	0	1	1	0	0	3
0	1	0	1	0	1	0	0	1	1	1	4
0	1	1	0	0	1	1	1	0	1	0	4
0	1	1	1	0	1	1	0	0	0	1	3
1	0	0	0	1	0	1	1	0	0	0	3
1	0	0	1	1	0	1	0	0	1	1	4
1	0	1	0	1	0	0	1	1	1	0	4
1	0	1	1	1	0	0	0	1	0	1	3
1	1	0	0	1	1	1	0	1	0	0	4
1	1	0	1	1	1	1	1	1	1	1	7
1	1	1	0	1	1	0	0	0	1	0	3
1	1	1	1	1	1	0	1	0	0	1	4

[D]= $[0\ 0\ 0\ 1]$ then D(X)=1 C(X)=D(X)g(X)=1.(X ³ +X+1)=X ³ +X+1	[C]=[0001011]
[D]=[0 0 1 0] then D(X)=X C(X)= X.(X^3 + X+1)= X^4 + X^2 +X	[C]=[0010110]

 $\begin{array}{l} [D] = [0 \ 0 \ 1 \ 1] \ \text{then} \ D(X) = X + 1 \\ C(X) = (X + 1).(\ X^3 + \ X + 1) = \\ X^3 + \ X + 1 + \ X^4 + \ X^2 + X = X^4 + \ X^3 + \ X^2 + 1 \\ \end{array}$

And so on with the rest of the codes.

b. Systematic cyclic codes:

The polynomial representation may be used with the same generator polynomial g(X) used in **non-Systematic** codes.

Procedure:

- 1. Find D(X) from [D]
- 2. Select g(X) of order r from factorization of $X^{n}+1$
- 3. $C(X) = X^r . D(X) + (\operatorname{Re} m \frac{X^r D(X)}{g(X)})$ where **Rem** is the reminder

of long division

4. Use
$$C(X)$$
 to find [C].

Note that C(X) consists of two parts, the first is $X^r.D(X)$ which is the same information data shifted to left by r position, the second is the reminder $\operatorname{Re} m \frac{X^r D(X)}{g(X)}$ of order (r-1) which is the r LSBs of the output code word or parity bits, hence [C] will have the form:

$$[C] = [a_1, a_2, \dots, a_k c_1, c_2, \dots, c_r]$$

Ex: find the code table for (7,4) systematic cyclic code generated by $g(X) = X^3 + X^2 + 1$

Sol:

a 1	\mathbf{a}_2	a3	a 4	c ₁	C ₂	C 3	Wi
0	0	0	0	0	0	0	
0	0	0	1	1	0	1	3
0	0	1	0	1	1	1	4
0	0	1	1	0	1	0	3
0	1	0	0	0	1	1	3
0	1	0	1	1	1	0	4
0	1	1	0	1	0	0	3
0	1	1	1	0	0	1	4
1	0	0	0	1	1	0	3
1	0	0	1	0	1	1	4
1	0	1	0	0	0	1	3
1	0	1	1	1	0	0	4
1	1	0	0	1	0	1	4
1	1	0	1	0	0	0	3
1	1	1	0	0	1	0	4
1	1	1	1	1	1	1	7

Here n=7, k=4, r=3

For [D]=[0001], D(X)=1

$$X^{r}.D(X) = X^{3}.1 = X^{3}$$

$$\frac{1}{X^{3} + X^{2} + 1} \frac{1}{X^{3}} \frac{X^{3} + X^{2} + 1}{X^{2} + 1}$$

 $C(X)=X^{r}D(X)+Reminder$ $=X^{3}+X^{2}+1$

Note that the reminder gives directly the r-parity bits if written in binary form.

For [D]=[0010], D(X)=X

$$X^{r}.D(X) = X^{3}.X = X^{4}$$
 $X^{3} + X^{2} + 1 X^{4}$
 $\frac{X^{4} + X^{3} + X}{X^{3} + X}$
 $\frac{X^{3} + X^{2} + 1}{X^{2} + X + 1}$

 $C(X) = X^4 + X^2 + X + 1$ [C]=[0010 111]

For [D]=[0011], D(X)=X+1

 $X^{r}.D(X) = X^{3}.(X+1) = X^{4}+X^{3}$


$$\frac{X+1}{X^{3} + X^{2} + 1 X^{4} + X^{3}}$$
$$\frac{X^{4} + X^{3} + X}{X}$$

 $C(X) = X^4 + X^3 + X$ [C]=[0011 010]

And so on with the rest of the codes

Implementation of Cyclic Encoder:

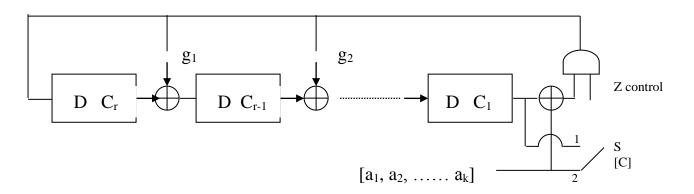Practically, the long division required in encoding is done using logic circuit. That implements the division by g(X) polynomial. In general : $g(X)=g_0+g_1X+g_2X^2+\ldots+g_rX^r$, then $g_0=g_r=1$ always for any factorization of X^n+1 . Hence only $g_1, g_2, \ldots, g_{r-1}$ is shown in the implementation circuit:



- This logic circuit is called Modular.
- Feedback shift register implemented using D-flip flop with synchronized clock.

Circuit Operation :-

Switch S is at position 1 giving the data bit to [C] output and at the same time for k clock pulses, the control Z is enabled "Z=1" to feedback the content to the registers to produce c_1, c_2, \ldots, c_r bits at the end of last clock.

Switch S is at position 2, the Z disabled to get these r parity bits to [C] and at the same time r 0's will be fed back to the register to initialize the register to the next data block.

NOTE

Previous encoding procedure for systematic cyclic code can be done faster without polynomial representation if instead of g(X) is converted into binary form called the "divisor" of the cyclic code.

Ex:

Using $g(X)=X^3+X^2+1$, find the output codeword for [D]=[0011] and [D]=[0010]

Sol:

- 1. Convert from polynomial into binary form $g(X) = X^3 + X^2 + 1$ [G]=[1101]
- 2. Add r 0's as LSB to data= $[a_1, a_2, ..., a_k]$ to get $[a_1, a_2, ..., a_k 0 \ 0 \ 0]$
 - for [D]=[0011] we will have [0011000]

```
3. Divide it by [G]
```

1	
1101)0011000	
001101	
000001	<u>0</u>

r-parity


Then [C]=[0011010]

For [D]=[0010]

The out put should be [C]=[0010111].. how??

Ex:

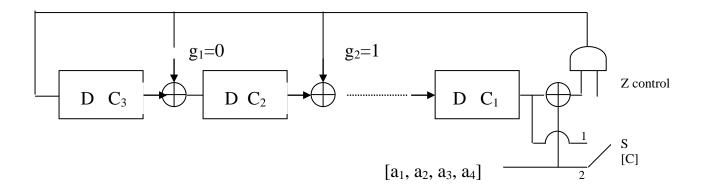Using the encoder logic circuit to find the o/p codeword for systematic cyclic code with $g(x) = X^3 + X^2 + 1$ and for [D]=[0101], [0010]



Sol:

First we write the transition equations for c_1 , c_2 , c_3 (we write the next state of them in terms of the present state and the input, this is done when Z=1 then:

$$c_{3}^{n+1} = c_{1}^{n} + a_{i}$$

$$c_{2}^{n+1} = c_{3}^{n}$$

$$c_{1}^{n+1} = c_{2}^{n} + c_{1}^{n} + a_{i} = c_{2}^{n} + c_{3}^{n+1}$$

For [D]=[0101]

1	a _i
	0
	1
	0
	1

c ₃	c_2	c_1
0	0	0
0	0	0
1	0	1
1	1	1
0	1	1
0	0	1
0	0	0
0	0	0

Then $c_1 c_2 c_3 = 110$ and [C]=[0101110]

For [D]=[0010]

a	i
C)
C)
1	-
C)

Then c₁ c₂ c₃=111 and [C]=[0010111]

c ₃	c_2	c_1
0	0	0
0	0	0
0	0	0
1	0	1
1	1	1
0	1	1
0	0	1
0	0	0

Decoding of Systematic Cyclic Code:-

At the receiver [R]=[C]+[E] where [E] is the error word Or R(X)=C(X)+E(X), E(X) is the error polynomial

Now if we divide above equation by g(X) taking the reminder :-

$$\operatorname{Re} m\left[\frac{R(X)}{g(X)}\right] = \operatorname{Re} m\left[\frac{C(X)}{g(X)}\right] + \operatorname{Re} m\left[\frac{E(X)}{g(X)}\right]$$

And since $\operatorname{Re} m\left[\frac{C(X)}{g(X)}\right] = 0$ as shown before, then :-
$$\operatorname{Re} m\left[\frac{R(X)}{g(X)}\right] = \operatorname{Re} m\left[\frac{E(X)}{g(X)}\right] = S(X) = \text{syndrome polynomial of order (r-1).}$$

- 1. If S(X) = 0 then no error occurs.
- 2. If S(X) # 0 then error occurs

To find the locations of these errors, the receiver may prepare a syndrome table, store it in its memory, use it to find [E] from [S] starting with less number of errors.

Ex: Prepare the syndrome table for (7,4) systematic cyclic code with $g(X)=X^3+X^2+1$ and for single error. Check the syndrome when double error at first and last positions occur.

Sol:-

	Error Word [E]							S_2	S ₃
0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	1	0	0	1
0	0	0	0	0	1	0	0	1	0
0	0	0	0	1	0	0	1	0	0
0	0	0	1	0	0	0	1	0	1
0	0	1	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	1	1
1	0	0	0	0	0	0	1	1	0
0	0	0	0	0	1	1	0	1	1
0	0	0	0	1	0	1	1	0	1

Forth Class	Electrical Dept.
Communication II	Nada Nasih

Each [S] is found from [E] by long division by g(X). for example if [E]=[0100000] error at second position from the left then:-

1	1	0	1	0	1	0	0	0	0	0
					1	1	0	1		
					0	1	0	1	0	
						1	1	0	1	
						0	1	1	1	0
							1	1	0	1
							0	0	1	1
									[S]	

Note that no repeated [S] for all possible single error. This is expected since w_{i(min)}=3 and the given (7,4) code is a single error correction. Note also for double error [E]=[0000011], then [S]=[011] which is single error at the second position (from the left), there by these errors cannot be corrected.

Now going back to the example for double error [E]=[1000001]

1	1	0	1	1	0	0	0	0	0	1	
				1	1	0	1				
				0	1	0	1	0			
					1	1	0	1			
					0	1	1	1	0		
						1	1	0	1		
						0	0	1	1	1	
								[S]			

[S]=[111] which is the same [S] as if single error occurs at third position from the left.

Ex: using previous syndrome table, find the corrected word for the received word [R]=[1010011].

Sol:-

First, the receiver will find [S] from the reminder of R(X)/g(X)

1	1	0	1	1	0	1	0	0	1	1
				1	1	0	1			
				0	1	1	1	0		
					1	1	0	1		
					0	0	1	1	1	1
							1	1	0	1
						0	0	0	1	0
									[S]	
	1	1 1	1 1 0	1 1 0 1	1	1 1 0 1 1	$ \begin{array}{cccccccccccccccccccccccccccccccccccc$	$ \begin{array}{cccccccccccccccccccccccccccccccccccc$	$ \begin{array}{cccccccccccccccccccccccccccccccccccc$	0 1 1 1 0


Hence, [S]=[010], using syndrome table and for this syndrome, [E]=[0000010] Then the corrected codeword

Then the corrected codeword

[C] = [R] + [E]1010011 $\underline{0000010}$ [C] = 1010001

Implementation of Cyclic Decoder:

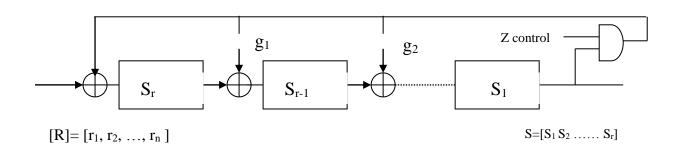
The long division of [R] by [G] to obtain the reminder is implemented is using logic circuit as shown for the generator g(X). The control Z is enabled for "n" clock pulses and then disabled for "r" clock pulses.



Forth Class	Electrical Dept.
Communication II	Nada Nasih

Ex: use the decoder circuit to find the syndrome and the corrected word for the received word [R]=[1011010], if $g(X)=X^3+X^2+1$

Sol:-

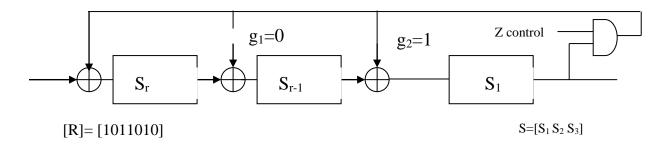

First we write the transition equations for $S_1 S_2 S_3$ when Z=1 :-

 $\begin{array}{l} S_{3}{}^{n+1} \!\!=\!\! S_{1}{}^{n} \!\!+\!\!r_{i} \\ S_{2}{}^{n+1} \!\!=\!\! S_{3}{}^{n} \\ S_{1}{}^{n+1} \!\!=\!\! S_{2}{}^{n} \!\!+\! S_{1}{}^{n} \end{array}$

\mathbf{r}_{i}	S ₃	S_2	\mathbf{S}_1
	0	0	0
1	1	0	0
0	0	1	0
1	1	0	1
1	0	1	1
0	1	0	0
1	1	1	0
0	0	1	1

Then [S]=[110], using the syndrome table then [E]=[1000000]. The corrected code word

 $[C] = \frac{1011010}{1000000}$